

3. Current Electricity

Extra Questions

Q.1 a) Which method should be used to connect the bulbs?

Ans. Parallel combination

b) What are the characteristics of this way of connecting the bulbs depending on the answer of A above ?

Ans.- a) The potential difference across each resistors is same.

b) The total current is equal to sum of currents through individual resistors.

c) The effective resistance of combination is less than any of the individual resistances.

d) The reciprocal of effective resistance of combinations equal to the sum of reciprocal of individual resistances.

e) The current through each resistor is inversely proportional to the resistance of the resistor.

f) This combination is used to decrease the resistance in circuit.

Q. 2 The following table shows current in Amperes and potential difference.

a) Find the resistance.

V (volts)	I (Amp)
4	9
5	11.25
6	13.25

$$1) R_1 = \frac{4V}{9A} = \text{about } 0.44 \Omega$$

$$R_2 = \frac{5V}{11.25A} = 0.44 \Omega$$

$$R_3 = \frac{6V}{13.5A} = 0.44 \Omega$$

Q.3 What will be the nature of the graph between the current and potential difference?

Ans- A straight line will be passing through the original (0,0)

Q.4 Match the pairs

1. Free electrons -	Increases the resistance in the circuit
2. Current -	V/R
3. Resistivity -	Weakly attached
4. Resistance in series	RA/L

Ans.-


1. Free electrons -	Weakly attached
2. Current -	V/R
3. Resistivity -	RA/L
4. Resistance in series	Increases the resistance in the circuit

Q. 5 The resistance of a conductor of length x is r. If its area of cross section is what is its resistivity? what is its unit ?

Ans- The notation for $R = \rho \frac{L}{A} \therefore$ Resistivity $\rho = \frac{RA}{L}$


$\therefore \rho \frac{ra}{x}$ unit : $\Omega \text{ m}$

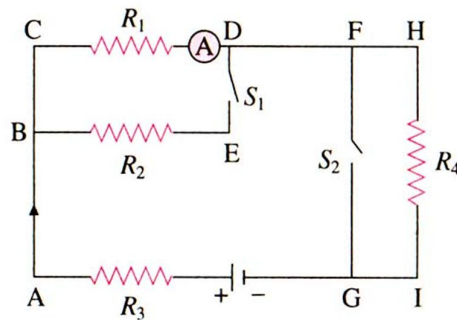Q.6 Resistances R_1 , R_2 , R_3 , and R_4 are connected as shown in the figure. S_1 and S_2 are two keys. Discuss the current flowing in the circuit in the following cases.



- 1) Both S_1 and S_2 are closed.
- 2) Both S_1 and S_2 are open.
- 3) S_1 is closed but S_2 is open.

Ans- 1) See the following figure.

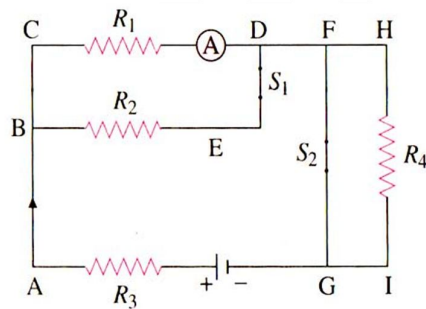

R_4 is shunted by an electric current by S_2 . Thus, the resistance of this combination will be zero.

R_1 and R_2 in parallel

$$\therefore \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\therefore R_p = \frac{R_1 R_2}{R_1 + R_2}$$

R_3 and R_p in series-

$$\therefore R_S = R_3 + R_{ap}$$

$$\therefore I_3 = \frac{V}{R_3 + R_S}$$

$$V_1 = V - I_3 R_3$$

$$= V - \frac{R_3 V}{R_3 + R_p} = V \left(1 - \frac{R_3}{R_3 + R_p} \right)$$


$$= V \left(\frac{R_p}{R_3 + R_p} \right)$$

$$\therefore I_1 = \frac{V_1}{R_1} = \frac{V}{R_1} \left(\frac{R_p}{R_3 + R_p} \right)$$

In the same way,

$$I_2 = \frac{V}{R_2} \left(\frac{R_p}{R_3 + R_p} \right)$$

2) See the following figure.

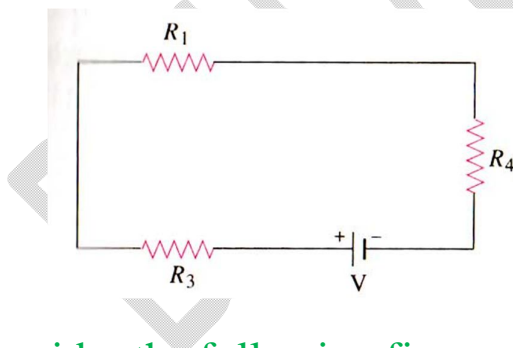


Consider the following figure

$$R_S = R_1 + R_3 + R_4$$

$$I = \frac{V}{R_1 + R_3 + R_4}$$

3) See the following figure

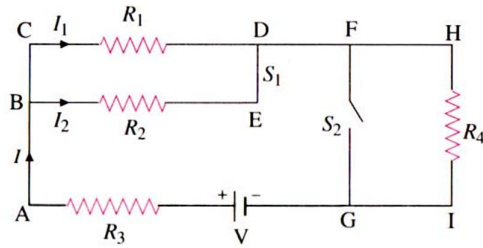

Consider the following figure

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_s = R_3 + R_4 + \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{V}{R_s} = I_3 = I_4$$

$$\text{Also, } I = I_1 + I_2 \text{ and } R_1 I_1 = R_2 I_2$$

$$\therefore I = I_1 + \frac{I_1 R_1}{R_2} \quad \therefore I_1 \left(1 + \frac{R_1}{R_2} \right) = I_1 \left(\frac{R_1 + R_2}{R_2} \right)$$

$$\therefore I_1 = \frac{R_2 I}{R_1 + R_2}, \quad I_2 = \frac{I_1 R_1}{R_2} = \frac{R_1}{R_2} \left(\frac{R_2 I}{R_1 + R_2} \right)$$

$$= \frac{R_1 I}{R_1 + R_2}$$

Q. 7 Three resistances x_1 , x_2 and x_3 are connected in a circuit in different ways, x is the effective resistance. The properties observed for these different ways of connecting x_1 , x_2 and x_3 are given below. Write the way in which they are connected in each case. (I – current, V – potential difference, x – effective resistance)

a) Current I flows through x_1 , x_2 , and x_3

Ans- Series combination, as resistances x_1 , x_2 and x_3 are in series and same current flows throughout them. This current is I .

b) x is large than x_1 , x_2 and x_3

Ans- The following resistances are connected in series the total x resistance. Is greater than each individual resistances.

c) x is smaller than x_1 , x_2 and x_3 .

Ans.- parallel combination.

d) The potential difference across x_1 , x_2 and x_3 is the same.

Ans.- Parallel combination.

e) $x = x_1 + x_2 + x_3$.

Ans.- series combination

$$f) x = \frac{1}{\frac{1}{x_1} + \frac{1}{x_2} + \frac{1}{x_3}}$$

Ans.- Parallel combination.

Q.8 The resistance of a 1m long nichrome wire is 6Ω . If we reduce the length of the wire to 70 cm, what will its resistance be?

Ans.- $R_1 = 6\Omega$, $R_2 = ?$, $L_1 = 1\text{m} = 100\text{cm}$, $L_2 = 70\text{cm}$

$R \propto L$ Hence we get that $R_1 \propto L_1$ and $R_2 \propto L_2$

We know that, $R = \rho \frac{L}{A}$

$$\therefore R_1 = \rho \frac{L_1}{A} \text{ and } R_2 = \rho \frac{L_2}{A}$$

Now, we get that $\frac{R_2}{R_1} = \frac{L_2}{L_1} = 0.7$

$$\therefore R_2 = 0.7 \times R_1 \text{ let us put the value of } R_1 = 0.7 \times 6\Omega \\ = 4.2 \Omega$$

The resistance will be 4.2Ω .

Q.9 When two resistors are connected in series, their effective resistance is 80Ω . When they are connected in parallel, their effective resistance is 20Ω . What are the values of the two resistances?

Ans- Let us consider two resistances as R_1 and R_2

Now $R_s = 80 \Omega$, as resistors are in series

$R_p = 20\Omega$, as resistors are in parallel

$$R_s = R_1 + R_2$$

$$\therefore R_1 + R_2 = 80, \text{ we get } R_2 = 80 - R_1$$

$$\text{Now, } \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \therefore \frac{1}{20} = \left(\frac{R_1 + R_2}{R_1 \cdot R_2} \right)$$

$$\therefore R_1 \cdot R_2 = 20 (R_1 + R_2)$$

$$\therefore R_1 (80 - R_1) = 20 (R_1 + 80 - R_1)$$

$$\therefore 80R_1 - R_1^2 = 1600$$

$$\therefore R_1^2 - 80R_1 + 1600 = 0$$

$$\therefore R_1^2 - 40R_1 - 40R_1 + 1600 = 0$$

$$\therefore R_1 (R_1 - 40) - 40 (R_1 - 40) = 0$$

$$\therefore (R_1 - 40) (R_1 - 40) = 0$$

$$\therefore R_1 - 40 = 0 \therefore R_1 = 40 \Omega$$

$$\therefore R_2 = 80 - R_1$$

Let us put the values of R_1 in given statement

$$\therefore R_2 = 80 - 40$$

$$\text{We get } R_2 = 40 \Omega$$

\therefore The two resistances are 40Ω and 40Ω .

Q. 10 If a charge of 420c flows through a conducting wire in 5 minutes, what is the value of current?

Ans- Let us consider the given data,

$Q = 420\text{c}$ and time $t = 5 \text{ mins}$,

Let us convert time in seconds

$$t = 5 \times 60 = 300\text{s}$$

We know that $I = \frac{Q}{t}$

$$= \frac{420}{300}$$

$$\therefore I = 1.4\text{A}$$

The value of the current is 1.4A .

Q. 11 What is an insulator?

Ans- The substances that have extremely high resistance are insulators.

Q. 12 To decrease the effective resistance in circuit, the resistance is connected in ____.

Ans- Parallel

Q. 13 Describe the magnitude of charge on one electron ?

Ans- The magnitude of charge on one electron is $1.6 \times 10^{-19}\text{C}$.

Q. 14 Describe the law proved in the experiment of electric current, potential difference and electric resistance. Explain it.

Ans.- Ohm's law is proved in the experiment of electric current, potential difference and electric resistance.

If the physical state of a conductor remains constant, current (I) flowing through it is directly proportional to the potential difference (V) between its two ends.

$$\text{i.e } I \propto V.$$

$$\therefore I = kV$$

$$\therefore I \times \frac{1}{k} = V$$

Where, $\frac{1}{k} = R = \text{Resistance of conductor.}$

$$I \times R = V$$

$$V = IR.$$

The physical state of a conductor includes length, area of cross section, temperature & material

Q. 15 Explain the function and working of a fuse.

Ans.- i) Fuse wire is used to protect domestic appliances.

ii) It is made of a mixture of substances and has a specific melting point.

iii) It is connected in series to the electric appliances. If for some reason, the current in the circuit increases excessively, the fuse wire gets heated and melts. The circuit gets broken and the flow of current stops, thus protecting the appliance.

Q. 16 Explain the expression for the resistors connected in parallel combination.

Ans.- a) Let R_1, R_2, R_3 are the resistors connected in parallel between points C and D, as in the diagram.

b) I_1, I_2, I_3 are the currents passing through resistors R_1, R_2 and R_3 .

c) Let 'v' is the potential difference between C and D.

Total current is –

$$I = I_1 + I_2 + I_3 \text{ ----- 1)}$$

d) Using ohm's law ----

$$I_1 = \frac{V}{R_1}, \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3} \text{ ----- 2)}$$

$$\text{And } I = \frac{V}{R_p}$$

Where R_p = equivalent resistance.

Putting the values of 2 and 3

$$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\ast V \left[\frac{1}{R_p} \right] = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\ast \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \text{ ----- 4)}$$

The above equation 4 is the equivalent resistance in parallel combination.

Let us consider, 'n' resistors in parallel,

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

Q. 17 Why does our body conduct electricity ?

Ans- Flow of charges and ions contain electric current. The body contains different types of ions as sodium, potassium, chloride etc, that have the property to conduct electricity.

Q. 18 Distinguish in Potential difference and Electric current.

Ans.-

Potential difference	Electric current
1) The difference in potential between positive and negative terminals of a cell.	1) The charge that is passing through a conductor in unit time.
2) Potential difference.	2) Electric current
$(V) = \frac{\text{work done (W)}}{\text{Charge (Q)}}$	$(I) = \frac{\text{charge (Q)}}{\text{Time (t)}}$
3) S.I unit is volt.	3) S.I unit is ampere.
4) Potential difference is measured by a voltmeter.	4) Electric current is measured by an ammeter.

Q. 19 A current of 0.34 A flows through a conductor, when a potential difference of 34V, is applied between its two ends, what is its resistance ?

Solution :- Potential difference (V) = 34V,

Current (I) = 0.34A, Resistance (R)

$$\ast R = \frac{V}{I}, R = \frac{34}{0.34} = 100\Omega.$$

\ast Resistance of the conductor = 100Ω .

Q. 20 Two identical wires made of two different materials are connected in series. If resistivities of the wires are in ratio 1:5 and resistance of first wire is 20Ω . Find the effective resistance of the combination?

$$\text{Solution- } \frac{P_1}{P_2} = \frac{1}{5}, R_1 = 20\Omega$$

$$R = P \frac{l}{A}, R_s = R_1 + R_2.$$

The wires are identical, l and A are the same for both the wires.

From the formula.

$$R \propto P$$

$$\ast \frac{R_1}{R_2} = \frac{P_1}{P_2} = \frac{1}{5}$$

$$\ast R_2 = 5R_1 = 5 \times 20 = 100\Omega$$

$$\ast R_s = 20 + 100 = 120\Omega$$

\ast We get, effective resistance of the combination is 120Ω .

Q. 21 Which substance does not allow current to flow through it?

Ans- An Insulator

Q. 22 What is the ratio of potential difference and current ?

Ans- Resistance

Q. 23 $1 \text{ mA} = \underline{\hspace{1cm}} \text{ A}$.

Ans- 10^{-3}

Q. 24 $1 \text{ microvolt} = \underline{\hspace{1cm}} \text{ volt}$.

Ans- 10^{-6}

Q. 25 What is the relation between ohm, volt and ampere ?

Ans- $1 \text{ ohm} = \frac{1 \text{ volt}}{1 \text{ ampere}}$

Q. 26 What is the relation between joule, coulomb and volt?

Ans- $1 \text{ volt} = \frac{1 \text{ J}}{1 \text{ C}}$

Q. 27 Define electric current.

Ans- Electric current is a flow of electrons in a conductor or amount of charge flowing through a particular cross sectional area in unit time.

Q. 28 What is an electric circuit?

Ans- A continuous path consisting of conducting wires, a switch or a plug key and other resistances, between the terminals of a battery or a cell along which an electric current flows is an electric circuit.

Q. 29 Describe a semi-conductor ?

Ans- A substance that works as an insulator under normal conditions, and behaves as a conductor under certain conditions is called semi-conductor.

E.g – Germanium

Q. 30 State the large units used for resistance.

Ans- $1 \text{ kilo ohm} = 10^3 \text{ ohms}$, $1 \text{ K}\Omega = 10^3 \Omega$.

$1 \text{ mega ohm} = 10^6 \text{ ohms}$, $1 \text{ M}\Omega = 10^6 \Omega$.

Q. 31 Why is electricity meter used?

Ans- The electricity meter measures the electric energy consumed. It is usually expressed in 'units', 1 unit = 1kilowatt- hour.

Q. 32 What safety measures will you take while using electricity.

Ans- 1) Every circuit should have electric fuse in proper working condition.

2) Periodically insulation of wires should be checked.

3) Electric appliances should have proper earthing.

4) Many electric appliances having high power should not be connected in same circuit.

5) With wet hands, electric appliances should never be handled.

Q. 33 Differentiate between Conductors and Insulators.

Ans.-

Conductors	Insulators
1) Conductors are the substances that have low resistances. Current flows with an ease in them.	1) Insulators are the substances that have extremely high resistance, and hence current does not easily flow through them.
2) Mostly they are metals.	2) They are mostly non-metals.
3) They contain large number of free electrons.	3) They do not contain any free electrons.

Q. 33 Differentiate between Resistance in series and Resistance in parallel.

Ans.-

Resistance in series	Resistance in Parallel
<p>1) The effective resistance of resistors is equal to the sum of their individual resistances. $R_s = R_1 + R_2 + R_3$.</p> <p>2) Same current flows through each resistor.</p> <p>3) The effective resistance is larger than each of the individual resistances.</p> <p>4) This arrangement is used to increase the resistance in circuit.</p>	<p>1) The inverse of effective resistance is equal to the sum of the inverses of the individual resistances. $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$</p> <p>2) The current flowing through each resistor is inversely proportional to its resistance. The total current in circuit, is the sum of the currents, flowing through each resistance.</p> <p>3) The effective resistance is smaller than each of the individual resistances.</p> <p>4) This arrangement is used to reduce the resistance in the circuit.</p>

Q. 34 Is the following statement true ?

A voltmeter is always connected in series in circuit.

Ans.- False

Q. 35 The direction of conventional current is from the positive end to the negative end of a cell state True or False.

Ans.- True.

Q. 36 A current of 0.5 A flows through conductor for 5 minutes. How much charge would have passed through conductor?

Ans.- Given $I = 0.5\text{A}$, $t = 5 \text{ minutes} = 300\text{s}$.

$$I = \frac{Q}{t}$$

$$Q = I \times t$$

$$= 0.5 \times 300$$

$$= 150\text{c.}$$

A charge of 150c passes through the conductor.

Q. 37 A current of 0.33A flows through a conductor, when a potential difference of 33v is applied between its two ends. What is its resistance?

Ans.- solution – $V = 33\text{v}$, $I = 0.33\text{ A}$

$$R = \frac{V}{I} = \frac{33}{0.33}$$

$$R = 100\Omega.$$

The resistance of the conductor is 100Ω .

Q. 38 If a charge of 450c, flows through a conducting wire in 5 minutes, what is the value of the current?

Ans- solution- $Q = 450\text{c}$, $t = 5 \times 60 = 300\text{s}$.

$$I = \frac{Q}{t}$$

$$= \frac{450}{300}$$

$$= 1.5\text{A}$$

$$\therefore I = 1.5\text{A}$$

Q. 39 The filament of an electric bulb has resistance of 600Ω . If a potential difference of 240V , is applied across, calculate the current flowing through it.

Ans- solution – $R = 600\Omega$, $V = 240\text{V}$.

By ohm's law, $I = \frac{V}{R}$

$$= \frac{240}{600} = 0.4 \text{ A.}$$

Q. 40 How will you prove that the unit of resistivity is $\Omega \text{ m}$?

Ans.- $R = \frac{\rho L}{A}$ $R = \text{Resistance } (\Omega)$

$\therefore \rho = \frac{RA}{L}$ $\rho = \text{Resistivity}$

$\therefore \rho = \frac{\Omega \text{m}^2}{L}$ $L = \text{Length of conductor (m)}$

$\therefore \rho = \Omega \text{m}$

$A = \text{Area of cross section of the conductor (m}^2\text{)}$

Q. 41 Define- one Ampere.

Ans- In a conductor, if one coulomb charge flows through it every second, the current is one Ampere.

Q. 42 Define – one ohm.

Ans- If one ampere current flows through a metallic conductor. When one volt potential difference is applied between its ends, then the resistance of the conductor is one ohm.

Q. 43 State ohm's law.

Ans- If the physical state of a conductor remains constant the current I flowing through it is directly proportional to the potential difference (v) between its two ends.

Q. 44 Why is a fuse always connected in series?

Ans- 1) Fuse stops the flow of excess of current, which prevents the damage to circuits and appliances. 2) The fuse is connected in series, so when current is passing through appliances, it passes through fuse.

Q. 45 Differentiate Voltmeter and Ammeter.

Ans.-

Voltmeter	Ammeter
1) This device measures the potential difference between two terminals of a cell.	1) This device measures the electric current flowing through a circuit.
2) It is connected in parallel with a cell.	2) It is connected in series with the cell.
3) It has very high resistance.	3) It has very low resistance.

Q. 46 Differentiate Resistance and Resistivity.

Ans.-

Resistance	Resistivity
1) The hindrance to the flow of electrons is called as Resistance.	1) Resistivity is the specific property of material of a conductor.
2) The S.I unit of resistance is ohm Ω .	2)The S.I unit of the resistivity is ohm- metre.
3) It depends upon temperature, length of conductor, area of cross section, material of conductor.	3) It depends on material of the conductor.

Q. 47 If three resistors $20\ \Omega$, $10\ \Omega$ and $5\ \Omega$ each are connected in series, what is the effective resistance in circuit?

Solution - $R_1 = 20\ \Omega$, $R_2 = 10\ \Omega$, $R_3 = 5\ \Omega$

Effective resistance in series = $R_s = ?$

$$R_s = R_1 + R_2 + R_3$$

$$= 20 + 10 + 5$$

$$= 35\ \Omega$$

Q. 48 Define – 1 volt.

Ans.- The potential difference between two points is said to be 1 volt if 1joule of work is done in moving 1coulomb of electric charge from one point to another.

$$1\text{ v} = \frac{1\text{J}}{1\text{C}}$$

Q. 49 The potential difference between any two points in a circuit is 60v. If a charge of 25c is transferred between these two points, find the work done in joules.

Ans.- 1500 joule.

Q. 50 If the T.V stops working, will the other appliances also stop working? Explain your answer.

Ans.- No, if the T.V stops working the other appliances will not stop working. Since the appliances are connected in parallel, even if T.V stops, the circuit does not break and the current flows through the other appliances.